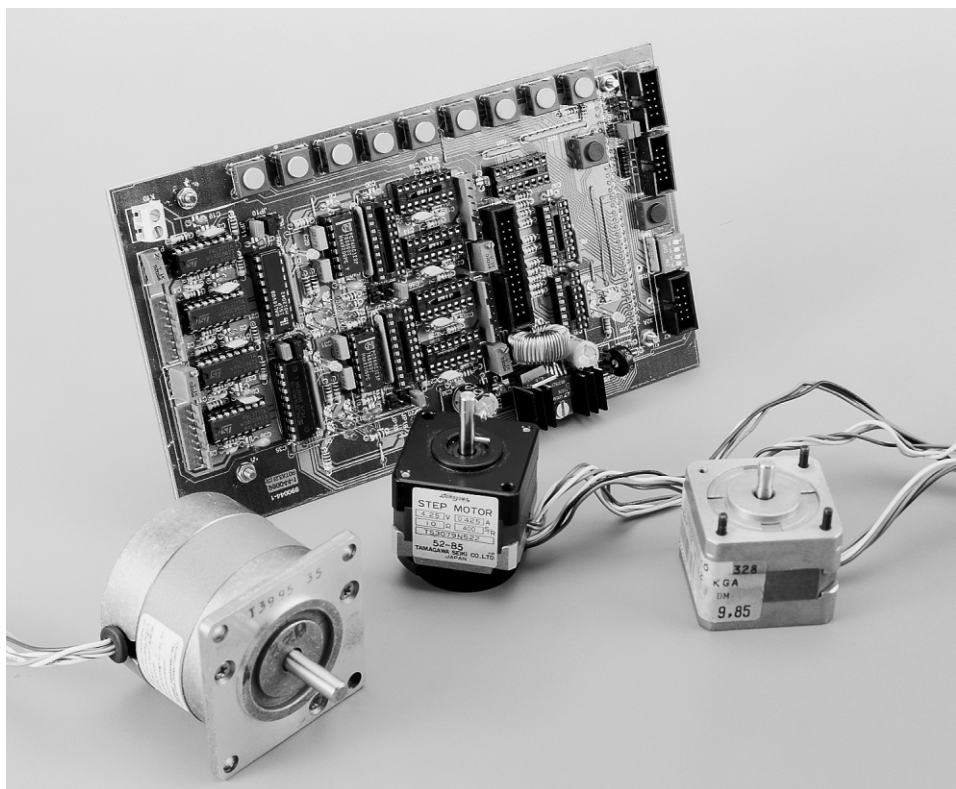


stepper motor control

part 2: SMC, a 80C166-powered driver for 4 motors

Over the past few years, we've witnessed a significant increase in the use of stepper motors. This result is largely due to technological advances and refinements achieved by the semiconductor industry, which currently offers a galaxy of integrated circuits, drivers and power stages specifically developed for the control of stepper motors. The number of ready-made controls complete with power drivers has also seen a remarkable increase.



Main features

- ◆ 4 power drivers, each having 2 bipolar output pairs for 0.5A or 1.2A phase winding current (PBL3717/PBL3717/2N)
- ◆ Current adjusted digitally in 3 steps, or analogue via presets
- ◆ Current reduction at no motor action
- ◆ Cut-off time 35 μ s
- ◆ Full and half-step operation, other modes available by reprogramming system GALs.
- ◆ LED indicators for clock and direction
- ◆ 4 optocoupler inputs for zeropoint sensors or contacts
- ◆ 8 optocoupler inputs for position sensors or contacts
- ◆ 2 serial interfaces
- ◆ 10 pushbuttons for manual control
- ◆ 1 reset pushbutton
- ◆ Power supply 12-40VDC, approx. 2.0A or 4.8A

The key advantage of using stepper motors is the ability to control motor speed and spindle position without the need for a closed control circuit. Drivers and power stages for stepper motors determine the amount of current and the direction of the current sent through the stepper motor windings. For spindle movement, the direction signal has to be complemented with a variable-frequency clock signal. For accurate positioning of the motor spindle, all pulses have to be counted and tallied. Clearly these functions challenge us to use a powerful microcontroller system like the 80C166 board described in the March & April 1999 issues of *Elektor Electronics*.

The Stepper Motor Control (SMC)

Design by K. H. Domnick

described in this article is the perfect mechanical end electrical companion to the 80C166 Evaluation System. The 80C166 employs tailor-made software to generate all the necessary signals for up to four power drivers on the motor control board, and also handles all information supplied by the available optocoupler inputs, the keyboard and the serial interface.

The construction, dimensions and mechanical assembly details of the 80C166 board and the SMC board are such that they can be housed together under a 42-TE wide front panel in a 19-inch case. The power supply is a simple one, turning the mains voltage into 12 to 40 volts d.c. (unregulated). Of course, the output current of the PSU should be adequate for the power drivers and stepper motors you want to use. A step-down voltage converter forms the 5-volt power supply for the HCMOS logic on the motor board.

The 80C166 board may also be used to provide clock signals to other stepper motor drivers, power stages and direction inputs. This however does require an additional regulated supply voltage of 5 V/300 mA for the board. Because all inputs and outputs are designed for TTL levels, level converters may be necessary where the board is connected to power drivers or sensors. Pushbuttons and a serial interface on the other hand may be directly connected.

Pushbuttons (Halt/Go) are provided to allow manual control of the stepper motors. As soon as the control becomes complex, however, you'll soon find that the necessary control signals have to be created with the aid of a PC.

THE HARDWARE IN DETAIL

The block diagram of the SMC (stepper motor control) is given in **Figure 1**. Each of the four (identical) power drivers consists of two stepper motor ICs type PBL3717 or PBL3717/2, a programmed GAL type 16V8 and one half of a re-triggerable monostable multivibrator type 74HC123. The output of the HC123 goes inactive when no clock signal is detected for 35-50 ms. This signal may be used to reduce the motor current when the spindle is not moving. The GAL, or rather its contents, determines the step order and current distribution through the windings — its outputs eventually lead to the two stepper motor ICs. These components, in turn, use just a handful of external components to generate the phase currents for the stepper motor windings. Their outputs toggle (change polarity) as a function of the TTL level applied to pin 8 (PH). Two other TTL inputs, pin 9 and pin 7 (I0 and I1) set up a comparator threshold of about 420 mV,

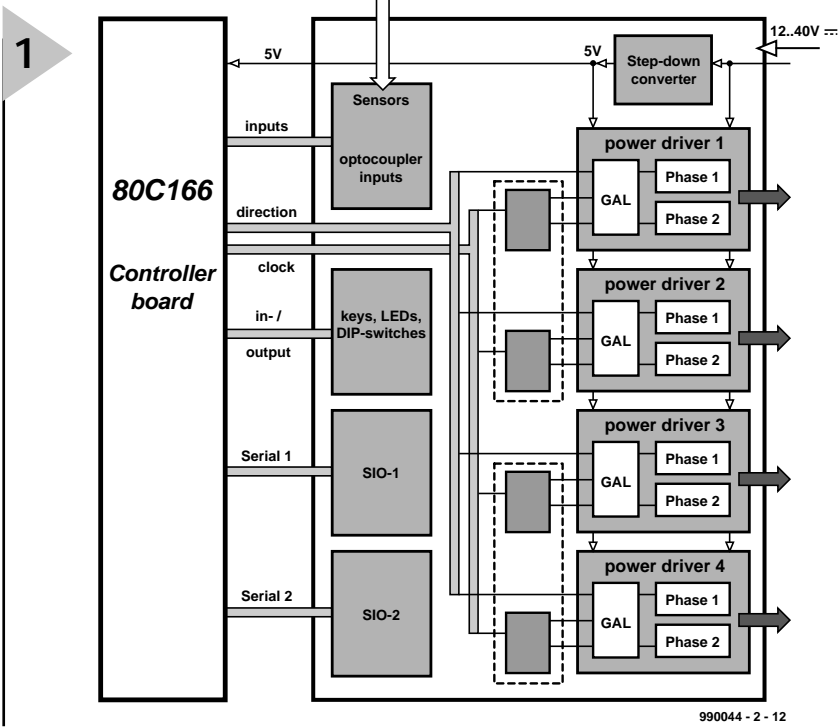


Figure 1. Block diagram of the stepper motor control. The program is hidden in blocks SIO1 and SIO2. The 80C166 microcontroller board supplies the necessary direction and clock information.

control inputs on the PBL3717 have to be held low with this method.

Three jumpers at the GAL inputs enable different step modes to be selected:

250 mV, 80 mV or 0 mV. When a coil current starts to flow, the resulting volt-

Jumper	GAL Pin	Function	open	closed
1	7	Step mode	Full step	Half step
2	8	Phase current	60%	100%
3	9	(Stand by)	(with Stand-by)	(w/o Stand-by)
		Stationary current	60%	100%

age drop across the 1-Ω resistor (Rx1/Rx5) at pin 16 is applied to input pin 10 of the comparator. When this voltage exceeds the set level, the comparator cuts off the current. After a 'cut-off' time of about 35 μs (determined by Rx3/Rx7 and Cx2/Cx4), the current flow is established again, and the process starts again.

The power stage will only supply enough current required to either build up or maintain the magnetic field in the phase winding. This is done because the high inductive coil reactance drops to the much lower ohmic resistance of the coil once the magnetic field has been established. Alternatively, this current may be adjusted with the aid of a potentiometer. The bias level set up by voltage dividers Rx4/Rx8 and Rx2/Rx6 is applied to the comparator input where it is effectively added to the voltage drop across the 1-Ω sense resistor that enables the comparator to cut the motor current. The disadvantage of this arrangement is that it is no longer possible to control the current distribution across the phase windings because all current

Other modes are possible by changing the GAL contents.

For zeropoint searching (spindle 'home' calibration) four optocoupler inputs are available for sensors or contact-less switches with a 'make' function. During a zeropoint search, the stepper motor first turns in the direction of a sensor. When this is actuated, the motor is halted for about 0.2 s. Next, the spindle is turned into the opposite direction until the sensor switches off again. The locating of the zeropoint is acknowledged, and the current motor position is defined as 'zero' or 'home'. When a stepper motor is connected up, you should take into account that the spindle will turn in the direction of the sensor during the zeropoint search.

The activation of one of the other 8 optocoupler inputs is reported individually. In this way, it is possible to detect certain states or when a certain position is reached.

The pushbuttons on the SMC front panel allow the stepper motors to be controlled by hand, as well as parameters to be entered. The preferred

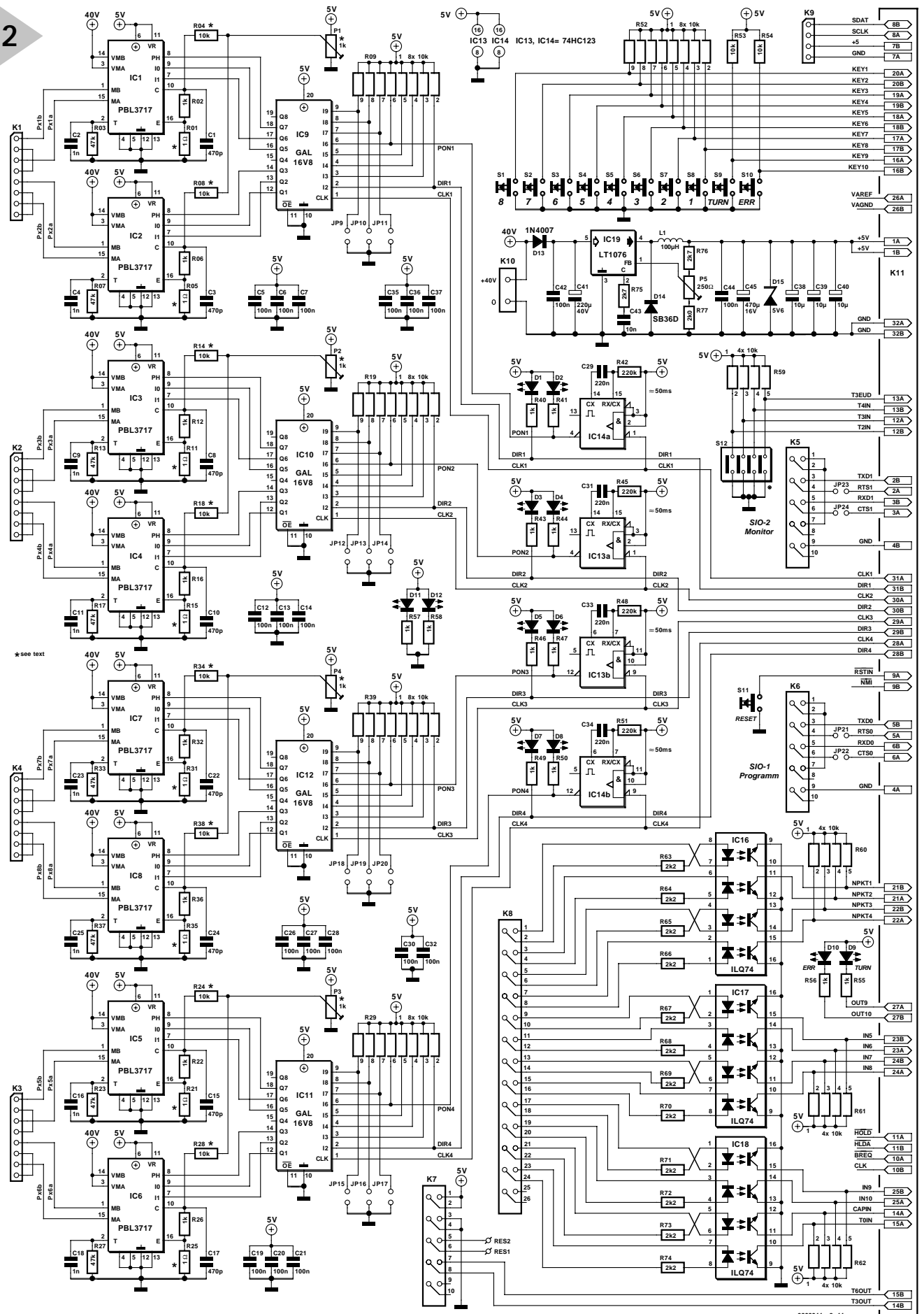


Figure 2. Complete circuit diagram of the stepper motor control (SMC). Individual circuit functions are clearly identifiable.

Connector pinouts



Function	Label	Pin (X1)		Pin (X1)	Label	Function
+5V pwr supply	+5V	1bc	1	2	1a	+5V pwr supply
O SIO 2 TxD Mon	P3.8 / TXD1	2bc	3	4	2a	P1.12 O SIO 2 RTS
I SIO 2 RxD Mon	P3.9 / RXD1	3bc	5	6	3a	P2.12/CC12IO I SIO 2 CTS
GND SIO 2	GND	4bc	7	8	4a	GND GND SIO 1
O SIO 1 TxD Prog	P3.10 / TXD0	5bc	9	10	5a	P1.11 O SIO 1 RTS
E SIO 1 RxD Prog	P3.11 / RXD0	6bc	11	12	6a	P2.11/CC11IO I SIO 1 CTS
+5V Serial	+5V	7bc	13	14	7a	GND GND Serial
I/O Serial Data	P1.10	8bc	15	16	8a	P2.10/CC10IO I/O Serial Clock
I (not used)	NMI#	9bc	17	18	9a	RSTIN# I Reset key
O 4	P3.15 / CLK	10bc	19	20	10a	P2.13/BREQ# O 1
O 2	P2.14/HLDA#	11bc	21	22	11a	P2.15/HOLD# O 3
I DIP switch Bit 4	P3.7 / T2IN	12bc	23	24	12a	P3.6 / T3IN I DIP switch Bit 3
I DIP switch Bit 2	P3.5 / T4IN	13bc	25	26	13a	P3.4 / T3EUD I DIP switch Bit 1
O Output T3	P3.3 / T3OUT	14bc	27	28	14a	P3.2 / CAPIN I Pos. Sensor 7
O Output T6	P3.1 / T6OUT	15bc	29	30	15a	P3.0 / T0IN I Pos. Sensor 8
I Key 10 (Cntrl)	P2.9 / CC9IO	16bc	31	32	16a	P2.8 / CC8IO I Key 9 (control)
I Key 8 (1)	P2.7 / CC7IO	17bc	33	34	17a	P2.6 / CC6IO I Key 7 (2)
I Key 6 (3)	P2.5 / CC5IO	18bc	35	36	18a	P2.4 / CC4IO I Key 5 (4)
I Key 4 (5)	P2.3 / CC3IO	19bc	37	38	19a	P2.2 / CC2IO I Key 3 (6)
I Key 2 (7)	P2.1 / CC1IO	20bc	39	40	20a	P2.0 / CC0IO I Key 1 (8)
I Motor zero SM-1	P5.0 / AN0	21bc	41	42	21a	P5.1 / AN1 I Motor zero SM-2
I Motor zero SM-3	P5.2 / AN2	22bc	43	44	22a	P5.3 / AN3 I Motor zero SM-4
I Pos. Sensor 1	P5.4 / AN4	23bc	45	46	23a	P5.5 / AN5 I Pos. Sensor 2
I Pos. Sensor 3	P5.6 / AN6	24bc	47	48	24a	P5.7 / AN7 I Pos. Sensor 4
I Pos. Sensor 5	P5.8 / AN8	25bc	49	50	25a	P5.9 / AN9 I Pos. Sensor 6
GND	VAGND	26bc	51	52	26a	VAREF +5V
O LED Cntrl	P1.9	27bc	53	54	27a	P1.8 A LED control
O Direction SM-4	P1.7	28bc	55	56	28a	P1.6 O Clock SM-4
O Direction SM-3	P1.5	29bc	57	58	29a	P1.4 O Clock SM-3
O Direction SM-2	P1.3	30bc	59	60	30a	P1.2 O Clock SM-2
O Direction SM-1	P1.1	31bc	61	62	31a	P1.0 O Clock SM-1
GND pwr supply	GND	32bc	63	64	32a	GND GND pwr supply

Function	Name	Pin (X2)		Pin (X2)	Name	Function
+5V pwr supply	+5V	1	1	2	6	+5V pwr supply
GND pwr supply	GND	2	3	4	7	GND GND pwr supply
Spare 2	Res 2	3	5	6	8	Res 1 Spare 1
Output T6	P3.1 / T6OUT	4	7	8	9	P3.3 / T3OUT Output T3
		5	9	10		-

(X2 is not normally used and provided for extensions)

Function	Name	Pin (X3)		Pin (X3)	Name	Function
	DTR / DSR0	1	1	2	6	DTR / DSR0
Output TxD1 Prog	P3.10 / TXD0	2	3	4	7	P1.11 Output RTS1
Input RxD1 Prog	P3.11 / RXD0	3	5	6	8	P2.11 / CC11IO Input CTS1
	DTR / DSR0	4	7	8	9	GND GND pwr supply
GND pwr supply	GND	5	9	10		-

Function	Name	Pin (X4)		Pin (X4)	Name	Function
	DTR / DSR1	1	1	2	6	DTR / DSR1
Output TxD2 Mon	P3.8 / TXD1	2	3	4	7	P1.12 Output RTS2
Input RxD2 Mon	P3.9 / RXD1	3	5	6	8	P2.12 / CC12IO Input CTS2
	DTR / DSR1	4	7	8	9	GND GND pwr supply
GND pwr supply	GND	5	9	10		-

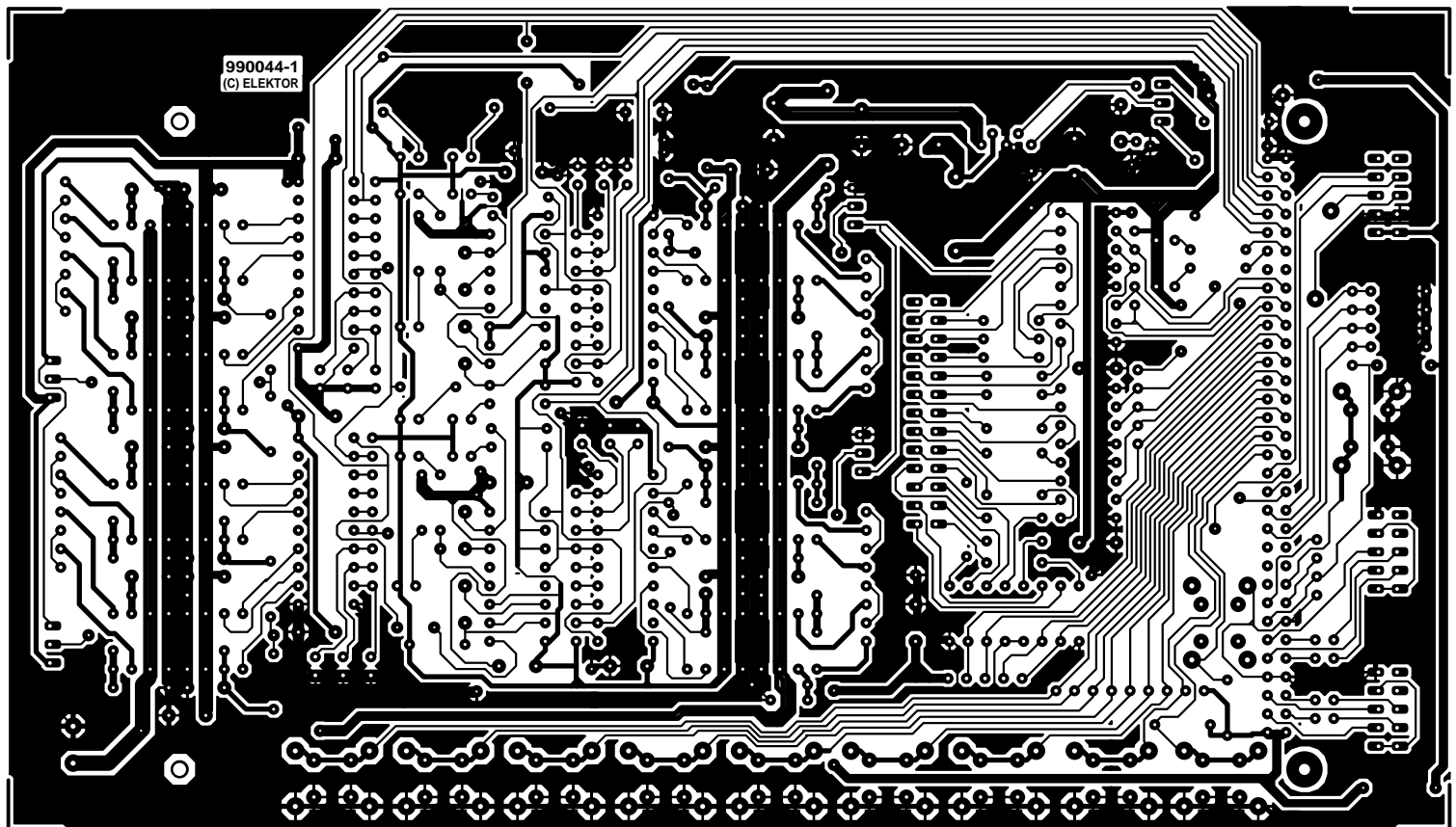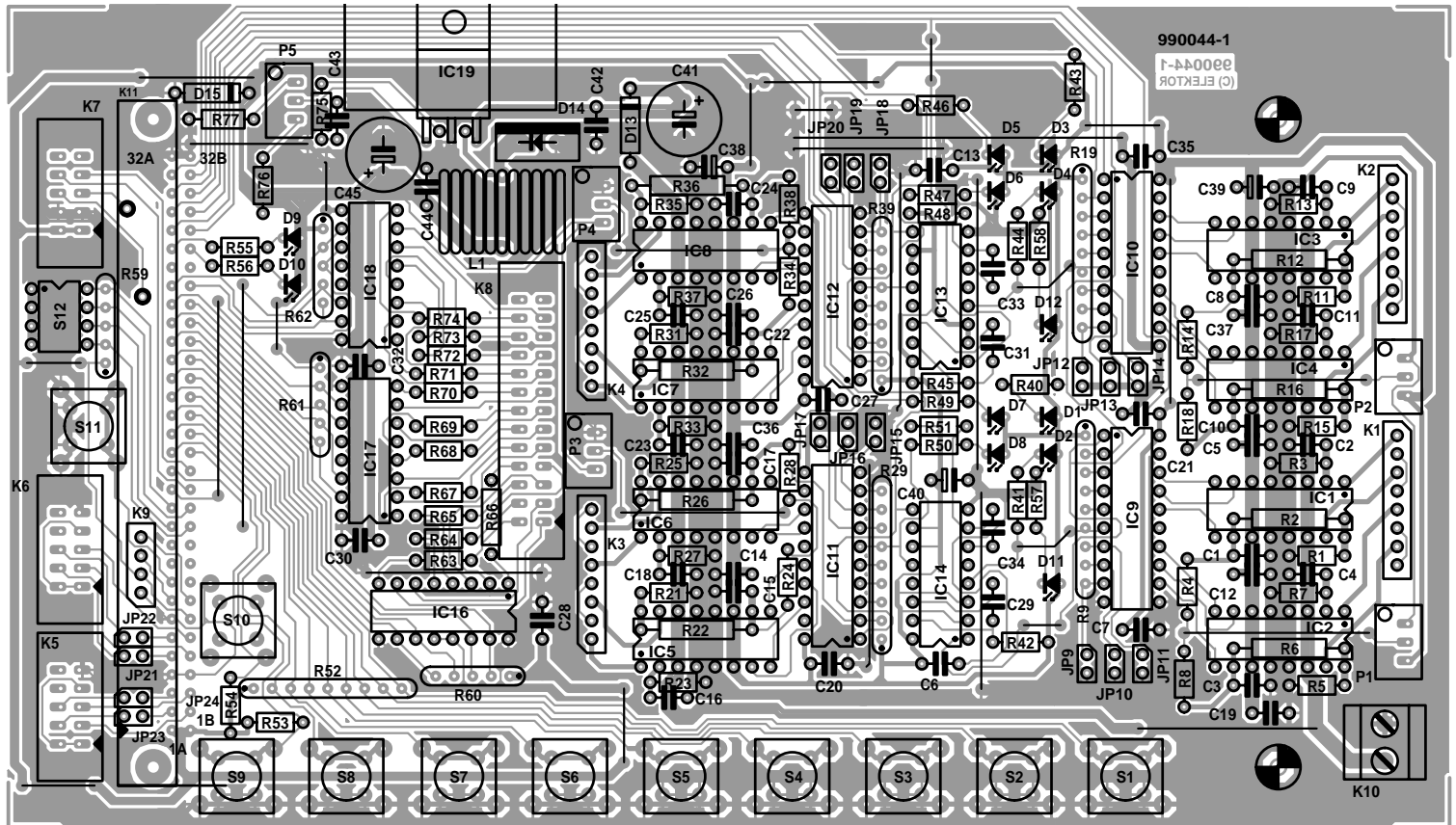

method of parameter inputting and control is however by means of the PC and its serial interface. The SMC is capable of reading parameters and commands via its serial input. The serial link is also used to return information to the PC.

WITH A HOT NEEDLE...

To build up the stepper motor control board you will need solder tin with a diameter of not more than 1 mm. The solder iron should have a fine bit and a tip temperature of about 340 degrees

Figure 3. Copper track layout and component mounting plan of the single-sided PCB designed for the SMC. Mechanically it is a perfect match to the 80C166 controller board.

COMPONENTS LIST

Resistors:

R1, R5, R11, R15, R21, R25, R31, R35 = 1Ω (1W for 1.2-A version)
 R2, R6, R12, R16, R22, R26, R32, R36, R40, R41, R43, R44, R46, R47, R49, R50, R55-R58 = 1kΩ
 R3, R7, R13, R17, R23, R27, R33, R37 = 47kΩ
 R4, R8, R14, R18, R24, R28, R34, R38, R53, R54 = 10kΩ
 R9, R19, R29, R39, R52 = 8×-way 10kΩ SIL array
 R10, R20, R30 = not used
 R42, R45, R48, R51 = 220kΩ
 R59-R62 = 4-way 10kΩ SIL array
 R63-R74 = 2kΩ
 R75, R76 = 2kΩ
 R77 = 2kΩ
 P1-P4 = 1kΩ multiturn preset, vertical, (top adjustment)
 P5 = 250Ω multiturn preset, vertical, (top adjustment)

Capacitors:

C1, C3, C8, C10, C15, C17, C22, C24 = 470pF
 C2, C4, C9, C11, C16, C18, C23, C25 = 1nF
 C5, C6, C7, C12, C13, C14, C19, C20, C21, C26, C27, C28, C30, C32, C35, C36, C37, C42, C44 = 100nF
 C29, C31, C33, C34 = 220nF
 C38, C39, C40 = 10μF 16V tantalum
 C41 = 220μF 40V
 C43 = 10nF
 C45 = 470μF 16V

Inductors:

L1 = 100μH 1A, max. dia. 15mm


Semiconductors:

D1-D8, D10 = LED, red
 D9 = LED, yellow
 D11, D12 = LED, green
 D13 = 1N4007
 D14 = SB360 or SB550 (Schottky diode, 3A)
 D15 = 5V6 1W zener diode
 IC1-IC8 = PBL3717A or PBL3717/2N (ST-Microelectronics)
 IC9-IC12 = GAL16V8 (order code 996524-1-a+b, 2 pcs)
 IC13, IC14 = 74HC123
 IC15 = not used
 IC16, IC7, IC18 = ILQ74
 IC19 = LT1076 CT

Miscellaneous:

JP1-JP8 = not used
 JP9-JP24 = jumper
 K1-K4 = 8-way PCB plug (Conrad Electronics o/n 741256)
 K5, K6, K7 = 10-way boxheader
 K8 = 26-way boxheader
 K9 = 4-way SIL header
 K10 = 2-way PCB terminal block
 K11 = 64-way pinheader
 S1-S11 = pushbutton, 1 make contact (ITT/Schadow PVA10AH2)
 S12 = 4-way DIP-switch
 Heatsink for voltage regulator
 PCB, order code 990044-1
 Disk (source code files), order code 996031-1
 On 80C166 board:
 H-EPROM = order code 996525-1
 L-EPROM = order code 996525-2

4

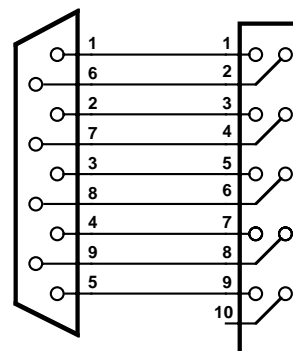

990044 - 2 - 13

Figure 4. A DIY cable adaptor.

also for flatcable mounting. Its 'schematic' is given in **Figure 4**.

The pinheader and the sub-D connector are aligned on the flatcable ends, clamped secure in a vise and then pressed on to the cable by slowly closing the vise. Do not forget the strain relief for the flatcable. On the pinheader, an arrow marks pin 1. Unused wires at either end of the cable may be cut off. A 26/25-way cable adaptor for the inputs is made in the same way.

Having read this instalment you have roughly a month to build the electronics. Next time, we will again tackle practical matters like taking the SMC in use and operating it. Faultfinding will also be discussed, as well as the operation of the system software developed by the author.

(990044-2)

Celsius. The wire jumpers being the 'components' with the lowest profile, they are first bent to shape, fitted and soldered. Next come the resistors, IC sockets, capacitors and so on, until all components are fitted except the integrated circuits, the pushbuttons and the LEDs. The step-down regulator IC is a tall component that has to be fitted flat on the board. Carefully insert its pins into the holes in the board, secure a small heatsink to it, and then solder the pins.

The connection to the 80C166 board is made via a 20-mm long pinheader at the solder side of the board. To make sure it fits correctly, insert the pinheader in the socket on the 80C166 board and secure the SMC board on top using four PCB spacers with a height of 20 mm. Next, fix the pinheader by soldering its corner pins and two centrally located pins. Finally you remove the controller board again and solder the remaining pins on the pinheader.

Next, concentrate on the pushbuttons and the LEDs. The pushbuttons are fitted with their caps mounted on them, and the LEDs, with spacers. Now mount the front panel on to the SMC board using four 15-mm high PCB spacers. The layout and drilling template of the front panel will be

given in next month's instalment. Check that no components are squashed between the board and the front panel! Once the LEDs and the pushbuttons are seated in their respective holes, their connecting terminals may be soldered.

A cable adapter is needed to enable the SMC to communicate with the outside world. It consists of piece of flatcable, an IDC-style 10-way pinheader and a 9-way sub-D socket,

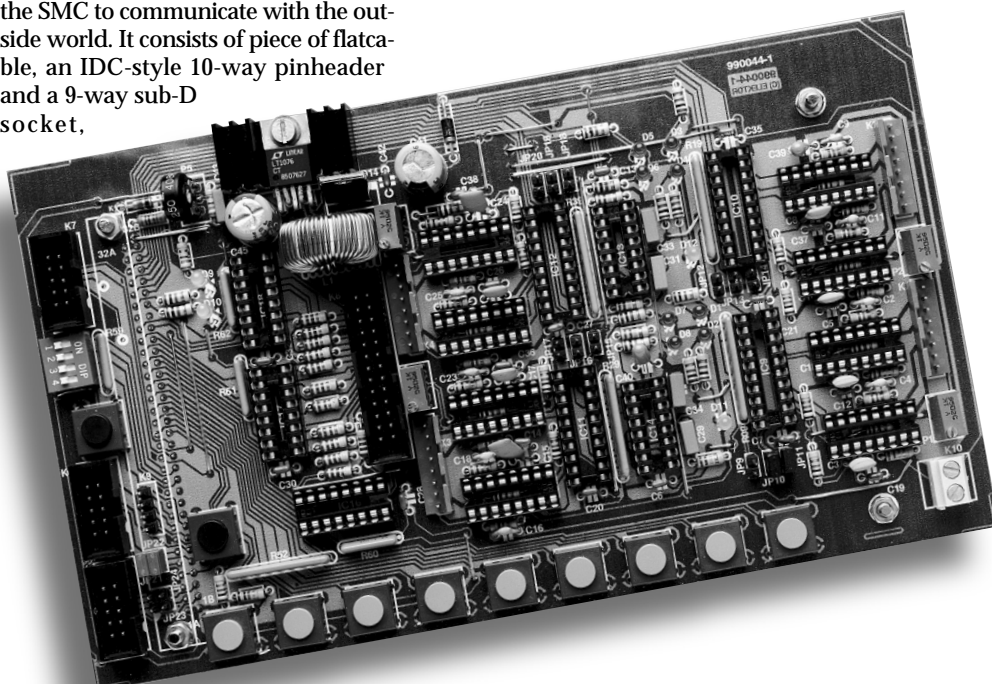


Figure 5. Completed prototype of the SMC board. Compare this carefully with your own work!